

AN-1201 APPLICATION NOTE

One Technology Way • P.O. Box 9106 • Norwood, MA 02062-9106, U.S.A. • Tel: 781.329.4700 • Fax: 781.461.3113 • www.analog.com

Software Configurable 12-Bit Dual-Channel Unipolar/Bipolar

Voltage Output Using the AD5722 DAC

CIRCUIT FUNCTION AND BENEFITS

This circuit provides unipolar and bipolar data conversion using the AD5722BREZ, a dual, 12-bit, serial input, unipolar/bipolar voltage output DAC and the REF192ESZ precision 2.5 V voltage reference. The only other external components needed for this 12-bit DAC circuit are decoupling capacitors on the supply pins and reference input, leading to savings in cost and board space. This circuit is well suited for closed-loop servo control applications.

CIRCUIT DESCRIPTION

Table 1. Devices Connected/Referenced

Product	Description
AD5722	Complete, dual, 12-bit, unipolar/bipolar voltage output DAC
REF192	Precision 2.5 V voltage reference

The AD5722 is a digital-to-analog converter that offers guaranteed 12-bit monotonicity, integral nonlinearity (INL) of ± 1 LSB, 0.1% total unadjusted error (TUE), and 10 μ s settling time. The AD5722 also integrates reference buffers and output amplifiers, which leads to further savings in both cost and board space. Performance is guaranteed over the following supply voltage ranges: AVDD supply range from +4.5 V to +16.5 V and AVSS supply range from -4.5 V to -16.5 V. AVSS can be connected to 0 V if only unipolar outputs are required.

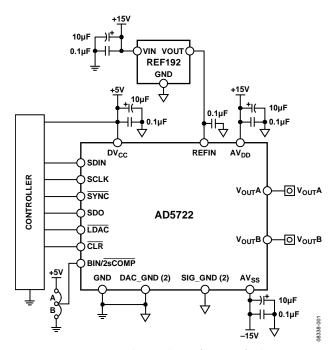


Figure 1. Unipolar /Bipolar Configuration for the AD5722 DAC (Simplified Schematic)

AN-1201 Application Note

The output range can be individually programmed for each output with these options: 0 V to +5 V, 0 V to +10 V, 0 V to +10.8 V, -5 V to +5 V, -10 V to +10 V, and -10.8 V to +10.8 V. The input coding is user selectable 2's complement or offset binary for a bipolar output (depending on the state of the BIN/2sCOMP pin). Coding is straight binary for a unipolar output. Figure 2 shows that the typical output error of this circuit at 25°C ambient temperature is less than 0.06 %FSR.

The circuit must be constructed on a multilayer PC board with a large area ground plane. Proper layout, grounding, and decoupling techniques must be used to achieve optimum performance (see MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of AGND and DGND* and MT-101 Tutorial, *Decoupling Techniques*).

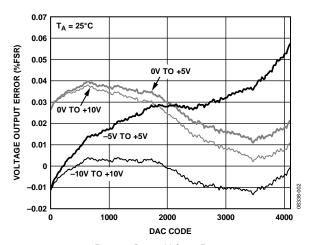


Figure 2. Output Voltage Error

LEARN MORE

Kester, Walt. 2005. *The Data Conversion Handbook*. Analog Devices. Chapters 3 and 7.

MT-015 Tutorial, *Basic DAC Architectures II: Binary DACs*. Analog Devices.

MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of AGND and DGND.* Analog Devices.

MT-101 Tutorial, Decoupling Techniques. Analog Devices.

Voltage Reference Wizard Design Tool.

Data Sheets and Evaluation Boards

AD5722 Data Sheet.

REF192 Data Sheet.

AD5754R Evaluation Board (Compatible with AD5722).

REVISION HISTORY

5/13—Rev. 0 to Rev. A

Changed Document Title from CN-0094 to

AN-1201Universal

7/09—Revision 0: Initial Version